

## Introduction

This report documents the design, simulation, synthesis, and testing of a two-digit BCD comparator system implemented on the Nexys A7 FPGA. The lab exercise required the design of registers, a comparator, validation logic, multiplexed seven-segment display drivers, and RGB LED outputs. The key learning outcomes included experience with structural VHDL, hierarchical design, SSD multiplexing, and on-board debugging. The final design was successfully tested on hardware with only minor implementation issues.

## Design Description

The design was implemented using a structural VHDL approach. The top-level block diagram is shown in Figure 1 below.

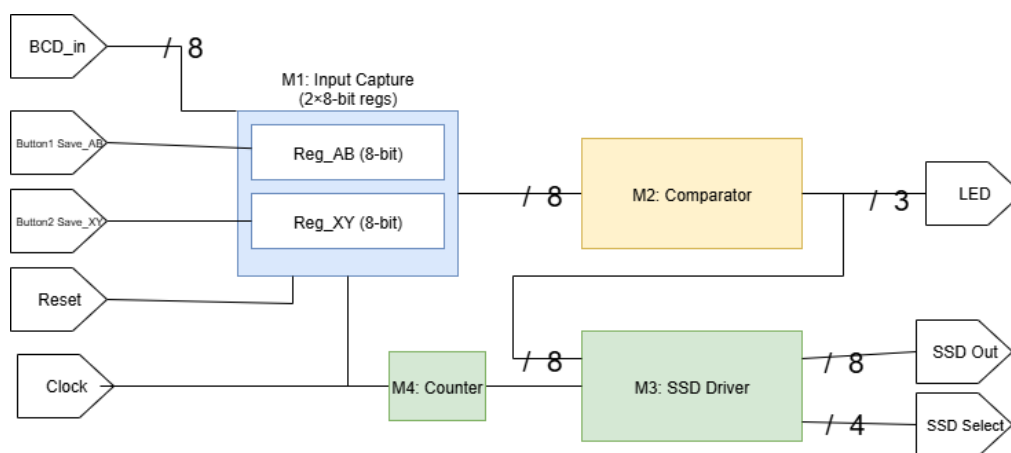


Figure 1 System Block Diagram

Each subsystem corresponds to a VHDL entity:

- EightBitReg: 8-bit register with clock enable and reset
- bcd\_validator: checks each 4-bit input for valid BCD (0–9)
- bcd\_comparator: compares two 8-bit BCD inputs and reports match type
- display\_controller: generates SSD digit outputs and RGB LED signals
- anode\_decoder: selects active SSD digit based on counter
- mux4x4: selects which digit to display
- hex\_to\_ssd\_const: maps hex digit to SSD cathode pattern

Which can be further looked at in the appendix (A-G).

As shown in Figure 1, the system has **four main inputs** and **three main outputs**:

### Inputs

- clk: the 100 MHz onboard system clock used for registers, counters, and SSD multiplexing.
- reset: active-high reset signal, clearing the registers and resetting the counter.
- btn1 and btn2: pushbuttons used as clock-enables for the registers, allowing values from the switches to be latched.

- switches[7:0]: eight onboard slide switches used to define the two BCD values (two digits each).

### Outputs

- ssd\_cathodes[6:0]: the seven cathode lines (A–G) for the multiplexed SSDs.
- ssd\_anodes[3:0]: the eight anode enable lines, of which only AN0–AN3 (the right-hand display) are active.
- rgb\_led[2:0]: a tri-colour LED indicating comparator results (e.g. red = no match, green = full match, yellow = partial match).

Each button (btn1, btn2) is connected to the enable input of one of the two registers, allowing the 8-bit value from the switches to be stored as BCD1 or BCD2. The registers reset to zero when reset is asserted, meaning that immediately after reset the RGB LED indicates a full match (green) and the SSDs display “HHHH” as both registers contain the same value.

Both the upper and lower digits of each register are passed through a validator to check whether the nibble is greater than 9, raising a flag if an invalid number is detected. The comparator takes the two 8-bit BCD values and produces match\_type (00 = no match, 01 = partial, 10 = full match) and digit\_matches (flags indicating which digits are equal), allowing the system to distinguish partial matches.

The display controller uses the comparator outputs and validator flags to generate the 4-digit output pattern. Valid BCD digits are displayed normally, invalid digits are shown as “E”, and matching digits may be replaced with “H”. The controller also drives the RGB LED colour according to the comparator results.

The digit counter divides the 100 MHz clock and generates a 2-bit count to cycle through the active SSD anodes, ensuring that all four digits are refreshed rapidly enough to appear simultaneously lit. The hex\_to\_ssd\_const module converts each 4-bit nibble into the active-low cathode pattern needed to drive the SSD, while the mux4x4 selects which digit is displayed on the SSD at each time step.

## Simulation Results

Simulation was performed in Vivado. Four scenarios were exercised: full match, partial match, no match, and reset. Because the SSD is multiplexed, the **anodes** (active-low) cycle through the four digits, while the **cathodes** (active-low A..G) show the segment pattern for whichever anode is currently active. In our mapping, the letter **H** corresponds to 0x48 on the 7-bit cathode bus (A..G).

### Full match - LED green, HHHH on SSD (Figure 2).

Both registers were set to 0x34. First, btn1 latched the switches into the A/B register; the RGB LED briefly appeared yellow while only one side was stored. When btn2 latched the same value into the X/Y register ( $\approx 15$  ms), the LED moved to **green**, indicating a full match. The cathodes hold at 0x48 as each anode is selected, so the multiplexed display reads **H H H H**.

 


Figure 2 Full match Simulation

### Partial match - LED yellow, matched digit shows H (Figure 3).

A/B was set to 0x35, then X/Y to 0x34. The LED moved to **yellow**, signalling a partial match (one digit equal). On the active anode slot for the matching digit the cathodes present **H** (0x48); on the non-matching slots they present the normal numeral patterns (e.g. 0x24 and 0x4C for “5” and “4” in this build). The result on the SSD is **H** over the equal digit and the original numerals elsewhere.

 


Figure 3 Half match Simulation

**No match - LED red, numerals ABXY on SSD (Figure 4).**

A/B was set to 0x12 and X/Y to 0x34. With no equal digits the LED remained **red** and each anode slot showed its corresponding numeral (e.g. a repeating sequence such as 0x06, 0x12, 0x4F, 0x4C for “1”, “2”, “3”, “4” per the chosen font).

 


Figure 4 No match Simulation

**Reset - registers cleared, LED green, HHHH on SSD (Figure 5).**

Asserting `reset` clears both 8-bit registers to 00. Because the numbers are identical after reset, the LED indicates **green** and all four digits display **H** (0x48 on the cathodes during each anode window).

 


Figure 5 Reset Simulation

## Synthesis/Implementation Results

After synthesising the design in Vivado, both the schematic views and the utilisation reports confirm that the system was implemented as expected. After synthesising the design in Vivado, both the schematic views and the utilisation reports confirm that the system was implemented as expected.

FigThe *RTL schematic* (Figure 6) clearly shows the modular structure of the top-level design. Each entity from the structural VHDL (two 8-bit registers, validators, comparator, display controller, digit counter, multiplexer, SSD decoder, and anode decoder) appears as a distinct block with the expected signal connectivity. The *synthesis schematic* (Figure 7) shows the lower-level netlist after synthesis, where each VHDL module is realised in terms of primitive flip-flops (FDREs), look-up tables (LUTs), and buffers. This view highlights how the abstract structural description is mapped onto the FPGA's fabric.

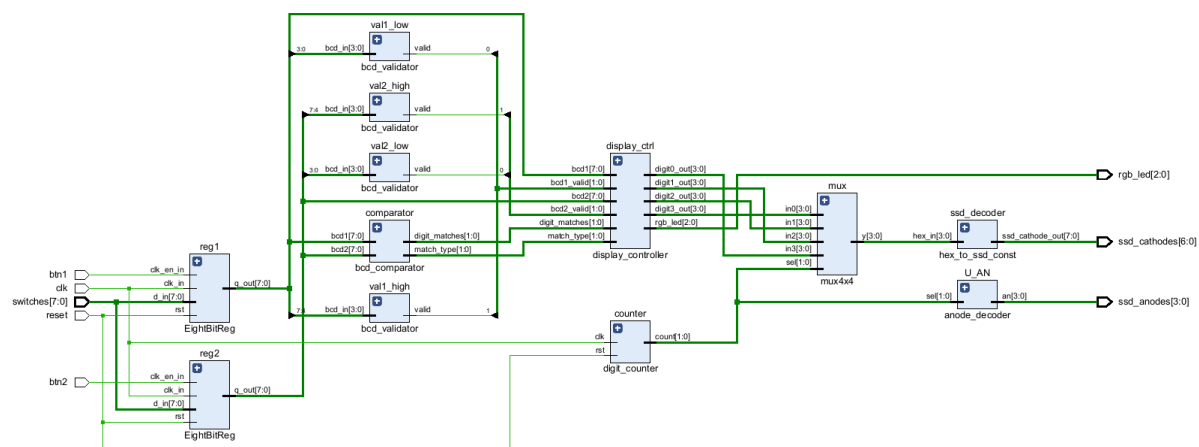


Figure 6 RTL schematic

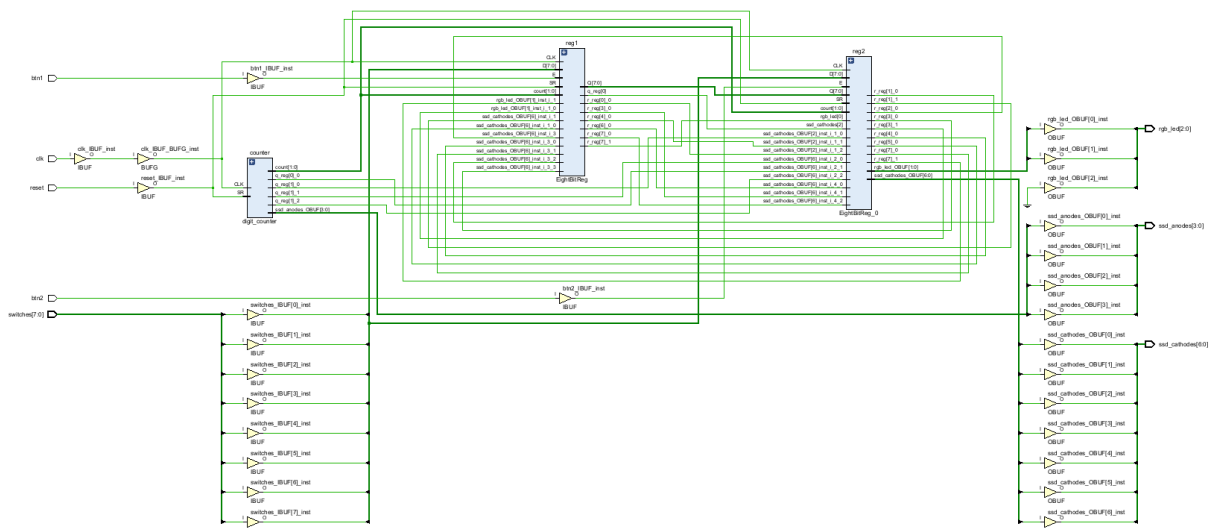


Figure 7 Synthesis Schematic

The primitive report (Figure 8) shows that the design uses 33 FDRE flip-flops, a collection of LUTs of various sizes, 1 BUFG for the system clock, and standard input/output buffers (IBUFs and OBUFs). The presence of CARRY4 elements reflects efficient implementation of arithmetic/comparison logic in the comparator and counter modules.

8. Primitives		
Ref Name	Used	Functional Category
FDRE	33	Flop & Latch
LUT6	25	LUT
OBUF	14	IO
IBUF	12	IO
LUT4	9	LUT
LUT3	9	LUT
LUT2	9	LUT
CARRY4	4	CarryLogic
LUT5	3	LUT
LUT1	1	LUT
BUFG	1	Clock

Figure 8 FPGA resource summary (Primitives table)

The utilisation by module (Figure 9) shows that the majority of LUTs are used in the two EightBitReg blocks and the comparator logic, while the counter consumes the largest share of registers (17 out of 33). This matches expectations, since the counter needs a bank of flip-flops to implement the scan divider, and the registers must each hold 8 bits of input data.

Name	Slice LUTs (63400)	Slice Registers (126800)	Bonded IOB (210)	BUFGCTRL (32)
bcd_comparator_top	44	33	26	1
counter (digit_counter)	9	17	0	0
reg1 (EightBitReg)	9	8	0	0
reg2 (EightBitReg_0)	26	8	0	0

Figure 9 Detailed Slice Logic Table

The utilisation summary (Figure 10) demonstrates that the design uses a negligible fraction of the available FPGA resources: The utilisation summary demonstrates that the design uses a negligible fraction of the available FPGA resources. The IO utilisation is higher in relative terms because the design makes heavy use of board peripherals (switches, push-buttons, LEDs, and SSD connections), but the overall logic utilisation is extremely low.

## Summary

Resource	Utilization	Available	Utilization %
LUT	44	63400	0.07
FF	33	126800	0.03
IO	26	210	12.38

 


Figure 10 Utilisation Summary Chart

## On-Board Testing

The design was tested on the Nexys A7 FPGA board. The right-hand four-digit SSD was used.

Testing confirmed that:

- Full match → LED green, both digits show H

 


Figure 11 Full match on board

- Partial match → LED yellow, only the matching digit shows H

 


Figure 12 Half match on board



- No match → LED red, digits show ABXY, where Y is a digit more than 9 showing “E”

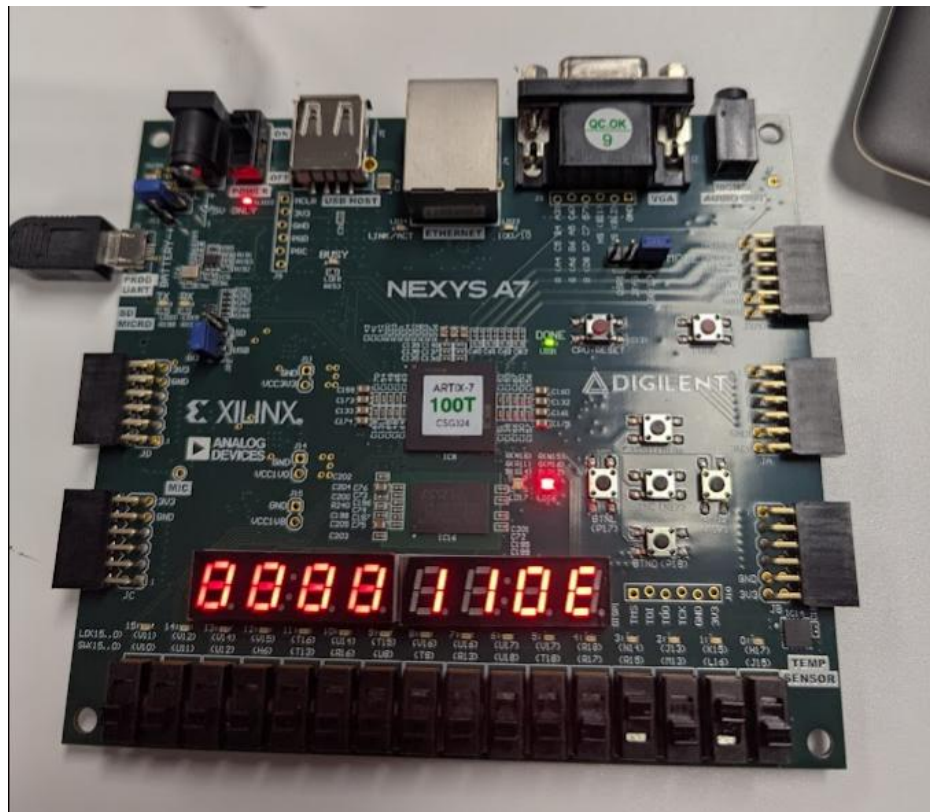


Figure 13 No match on board

- Reset clears registers

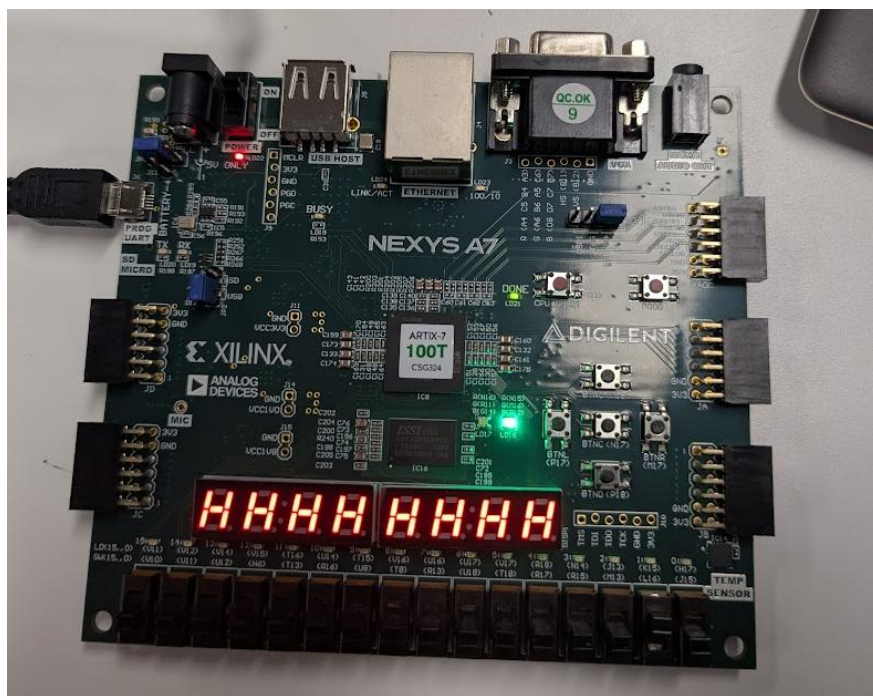


Figure 14 Reset on board



## Discussion and Conclusion

The lab successfully demonstrated the use of a modular VHDL design to implement a multi-component digital system. By structuring the system into separate entities such as registers, validators, comparator, display controller, multiplexer, and SSD decoder the design process was simplified and each module could be independently developed, simulated, and tested. This modular approach aligns with good hardware engineering practice and reflects how large FPGA designs are normally partitioned.

Several challenges were encountered and resolved during development. One challenge was the correct ordering of SSD digits: the logical digit outputs from the controller did not initially align with the physical anode scan order, which caused characters to appear scrambled across the display. This was resolved by deliberately cross-mapping the multiplexer inputs so that each digit was displayed in the intended position. Another issue was the mapping of the RGB LED bits, where red/green/blue ordering needed to be confirmed against the board documentation to ensure that “green” for a full match and “yellow” for partial match displayed as expected. A further practical challenge was the presence of two banks of SSD anodes on the Nexys A7; only the right-hand bank (AN0–AN3) was used, while the left-hand bank remained unused but was initially being unintentionally driven.

In addition, the reset functionality can be refined. In the current implementation, asserting reset clears both registers to zero, which causes the LED to indicate a full match (green) and all SSD digits to display “H”. A more intuitive behaviour would be for reset to instead drive the LED red to indicate “no data loaded”, while simultaneously blanking the SSD cathodes to ensure no misleading characters are displayed. This change would make the system state on reset clearer to the user. Furthermore, the unused left-hand SSD bank should be explicitly disabled so that it remains blank at all times, improving clarity and avoiding potential confusion during demonstrations.

In conclusion, the design met its functional requirements by correctly detecting full, partial, and no matches, driving the RGB LED and SSD outputs accordingly. The lab reinforced practical FPGA skills in structural modelling, simulation, and hardware verification. The suggested improvements enhanced reset behaviour, explicit disabling of unused SSD digits, debouncing of inputs, and scalability of the comparator represent natural next steps that would increase robustness, usability, and reusability of the system.

## References

Chat-GPT was used to guided me through coding, debugging, and report writing, with particular emphasis on SSD multiplexing and digit alignment, simulation best practices in Vivado, and clearer documentation and report structure.

<https://chatgpt.com/share/68aae1b7-cd5c-8009-a377-91558378b06d>

## Appendix

### A – Eight bit register VHDL description

```
34 entity EightBitReg is
35     port (
36         d_in      : in  std_logic_vector(7 downto 0);
37         clk_in     : in  std_logic;
38         clk_en_in  : in  std_logic;
39         rst        : in  std_logic;                -- active-high, synchronous
40         q_out      : out std_logic_vector(7 downto 0)
41     );
42 end EightBitReg;
43
44 architecture Behavioral of EightBitReg is
45     signal r : std_logic_vector(7 downto 0) := (others => '0');
46 begin
47     process(clk_in)
48     begin
49         if rising_edge(clk_in) then
50             if rst = '1' then
51                 r <= (others => '0');                -- clear register
52             elsif clk_en_in = '1' then
53                 r <= d_in;                          -- latch input
54             end if;
55         end if;
56     end process;
57
58     q_out <= r;
59 end Behavioral;
```

### B – bcd Validator VHDL description

```
5 entity bcd_validator is
6     Port (
7         bcd_in : in STD_LOGIC_VECTOR (3 downto 0);
8         valid  : out STD_LOGIC
9     );
10 end bcd_validator;
11
12 architecture Behavioral of bcd_validator is
13 begin
14     process(bcd_in)
15     begin
16         if unsigned(bcd_in) <= 9 then
17             valid <= '1';
18         else
19             valid <= '0';
20         end if;
21     end process;
22 end Behavioral;
```

## C – bcd Comparator VHDL description

```
4 entity bcd_comparator is
5     Port (
6         bcd1 : in STD_LOGIC_VECTOR (7 downto 0); -- First 2-digit BCD (AB)
7         bcd2 : in STD_LOGIC_VECTOR (7 downto 0); -- Second 2-digit BCD (XY)
8         match_type : out STD_LOGIC_VECTOR (1 downto 0); -- 00=no match, 01=partial, 10=full
9         digit_matches : out STD_LOGIC_VECTOR (1 downto 0) -- bit 1: high digit match, bit 0:
10    );
11 end bcd_comparator;
12
13 architecture Behavioral of bcd_comparator is
14     signal high_digit_match, low_digit_match : STD_LOGIC;
15 begin
16     -- Compare high digits (A vs X)
17     high_digit_match <= '1' when bcd1(7 downto 4) = bcd2(7 downto 4) else '0';
18
19     -- Compare low digits (B vs Y)
20     low_digit_match <= '1' when bcd1(3 downto 0) = bcd2(3 downto 0) else '0';
21
22     digit_matches <= high_digit_match & low_digit_match;
23
24     -- Determine match type
25     process(high_digit_match, low_digit_match)
26     begin
27         if high_digit_match = '1' and low_digit_match = '1' then
28             match_type <= "10"; -- Full match
29         elsif high_digit_match = '1' or low_digit_match = '1' then
30             match_type <= "01"; -- Partial match
31         else
32             match_type <= "00"; -- No match
33         end if;
34     end process;
35 end Behavioral;
```

## D – Anode decoder VHDL description

```
34 entity anode_decoder is
35     port (
36         sel : in std_logic_vector(1 downto 0);
37         an : out std_logic_vector(3 downto 0) -- active-low
38     );
39 end;
40
41 architecture rtl of anode_decoder is
42 begin
43     with sel select
44         an <= "1110" when "00",
45             "1101" when "01",
46             "1011" when "10",
47             "0111" when others;
48 end;
```

## E – Display Controller VHDL description

```
20 architecture Behavioral of display_controller is
21     constant H_PATTERN : STD_LOGIC_VECTOR(3 downto 0) := "1111"; -- Use F to represent 'H'
22     constant E_PATTERN : STD_LOGIC_VECTOR(3 downto 0) := "1110"; -- Use E for error
23 begin
24     process(bcd1, bcd2, match_type, digit_matches, bcd1_valid, bcd2_valid)
25     begin
26         -- Default RGB LED to red
27         rgb_led <= "001"; -- Red
28
29         -- Check for invalid BCD inputs
30         if bcd1_valid /= "11" or bcd2_valid /= "11" then
31             -- Error case - show 'E' for invalid digits
32             rgb_led <= "001"; -- Red
33             -- Show E for invalid digits, actual digits for valid ones
34             if bcd1_valid(1) = '0' then
35                 digit3_out <= E_PATTERN;
36             else
37                 digit3_out <= bcd1(7 downto 4);
38             end if;
39
40             if bcd1_valid(0) = '0' then
41                 digit2_out <= E_PATTERN;
42             else
43                 digit2_out <= bcd1(3 downto 0);
44             end if;
45
46             if bcd2_valid(1) = '0' then
47                 digit1_out <= E_PATTERN;
48             else
49                 digit1_out <= bcd2(7 downto 4);
50             end if;
51
52             if bcd2_valid(0) = '0' then
53                 digit0_out <= E_PATTERN;
54             else
55                 digit0_out <= bcd2(3 downto 0);
56             end if;
57
58         else
59             -- Valid BCD inputs
60             case match_type is
61                 when "10" => -- Full match
62                     rgb_led <= "010"; -- Green
63                     digit3_out <= H_PATTERN;
64
65                     digit2_out <= H_PATTERN;
66                     digit1_out <= H_PATTERN;
67                     digit0_out <= H_PATTERN;
68
69                 when "01" => -- Partial match
70                     rgb_led <= "011"; -- Yellow (red + green)
71                     -- Show H for matching digits, actual digits for non-matching
72                     if digit_matches(1) = '1' then
73                         digit3_out <= H_PATTERN; -- A matches X
74                         digit1_out <= H_PATTERN;
75                     else
76                         digit3_out <= bcd1(7 downto 4); -- Show A
77                         digit1_out <= bcd2(7 downto 4); -- Show X
78                     end if;
79
80                     if digit_matches(0) = '1' then
81                         digit2_out <= H_PATTERN; -- B matches Y
82                         digit0_out <= H_PATTERN;
83                     else
84                         digit2_out <= bcd1(3 downto 0); -- Show B
85                         digit0_out <= bcd2(3 downto 0); -- Show Y
86                     end if;
87
88                 when others => -- No match
89                     rgb_led <= "001"; -- Red
90                     digit3_out <= bcd1(7 downto 4); -- A
91                     digit2_out <= bcd1(3 downto 0); -- B
92                     digit1_out <= bcd2(7 downto 4); -- X
93                     digit0_out <= bcd2(3 downto 0); -- Y
94             end case;
95         end if;
96     end process;
97 end Behavioral;
```

## F – 4x4 Mux VHDL description

```
34 entity mux4x4 is
35     port (
36         in3,in2,in1,in0 : in  std_logic_vector(3 downto 0);
37         sel               : in  std_logic_vector(1 downto 0);
38         y                 : out std_logic_vector(3 downto 0)
39     );
40 end;
41
42 architecture rtl of mux4x4 is
43 begin
44     with sel select y <=
45         in3 when "00",
46         in2 when "01",
47         in1 when "10",
48         in0 when others; -- "11"
49 end;
```

## G – Hex to ssd VHDL description

```
40
41 architecture Dataflow of hex_to_ssd_const is
42     subtype cathode_out_t is std_logic_vector(7 downto 0); -- [7]=A ... [0]=DP
43
44     -- ACTIVE-LOW patterns for common-anode displays:
45     -- These match the usual "segments on = 0", and bit order A..G..DP.
46     constant ZERO : cathode_out_t := B"0000_0011";
47     constant ONE  : cathode_out_t := B"1001_1111";
48     constant TWO  : cathode_out_t := B"0010_0101";
49     constant THREE : cathode_out_t := B"0000_1101";
50     constant FOUR  : cathode_out_t := B"1001_1001";
51     constant FIVE  : cathode_out_t := B"0100_1001";
52     constant SIX   : cathode_out_t := B"0100_0001";
53     constant SEVEN : cathode_out_t := B"0001_1111";
54     constant EIGHT : cathode_out_t := B"0000_0001";
55     constant NINE  : cathode_out_t := B"0001_1001";
56     constant EE    : cathode_out_t := B"0110_0001"; -- 'E'
57     constant HH    : cathode_out_t := B"1001_0001"; -- 'H' (segments B, C, E, F, G on)
58 begin
59     ssd_cathode_out <=
60         ZERO when hex_in = X"0" else
61         ONE  when hex_in = X"1" else
62         TWO  when hex_in = X"2" else
63         THREE when hex_in = X"3" else
64         FOUR  when hex_in = X"4" else
65         FIVE  when hex_in = X"5" else
66         SIX   when hex_in = X"6" else
67         SEVEN when hex_in = X"7" else
68         EIGHT when hex_in = X"8" else
69         NINE  when hex_in = X"9" else
70         EE    when hex_in = X"E" else
71         HH    when hex_in = X"F" else -- 'H' pattern for hex value F
72         (others => '1');
73 end Dataflow;
74
```